

# HVDC GRID PROTECTION

Dr Fainan Hassan  
Head of NTI, HVDC

TU Delft – workshop  
Power System Integrity – Bring AC and DC together  
07/02/2024

# Outlines

- Introduction
- AC protection approach to HVDC
- New protection requirements for HVDC grids
- DC protection approach to HVDC grids
- DCCB operating principle
- System impacts on DCCB design
- Conclusions

# Introduction

DC grids are emerging as a technology “natural selection” due to co-location of new loads and generation and requirements for cost effective solutions esp offshore

- Ambitious targets for offshore wind (and wave) capacity esp. in Europe by 2050
- Electrification of oil and gas platforms
- Hydrogen production for clean maritime


Elemental research and development work has been done during the last decade

- DCCB demonstrators – GE DCCB prototype as part of EC project Twenties in 2013

Today – it’s “System of Systems” time



# AC protection approach to HVDC


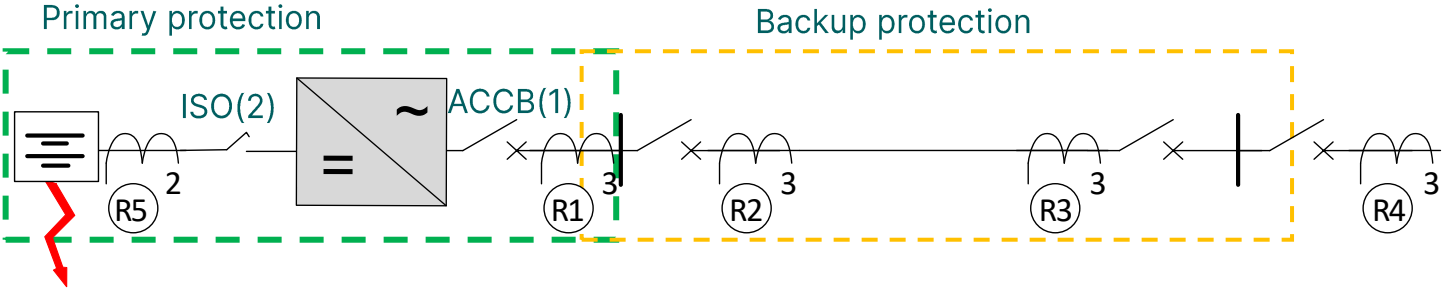


```
graph LR; A[Detect the fault (R5)] --> B[Block converter]; B --> C[Trip ACCB (1)]; C --> D[Isolate the fault (ISO(2))]; D --> E[Reclose ACCB (1)]; E --> F[Deblock converter];
```

Assuming converter can operate as STATCOM in this example
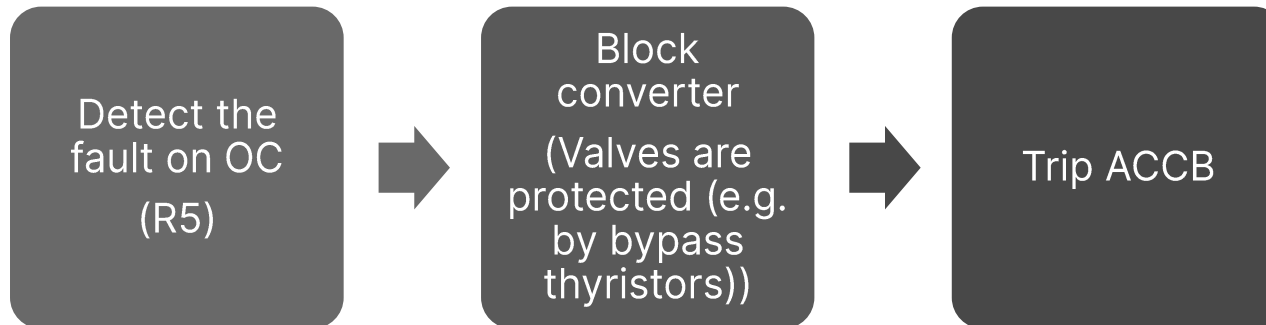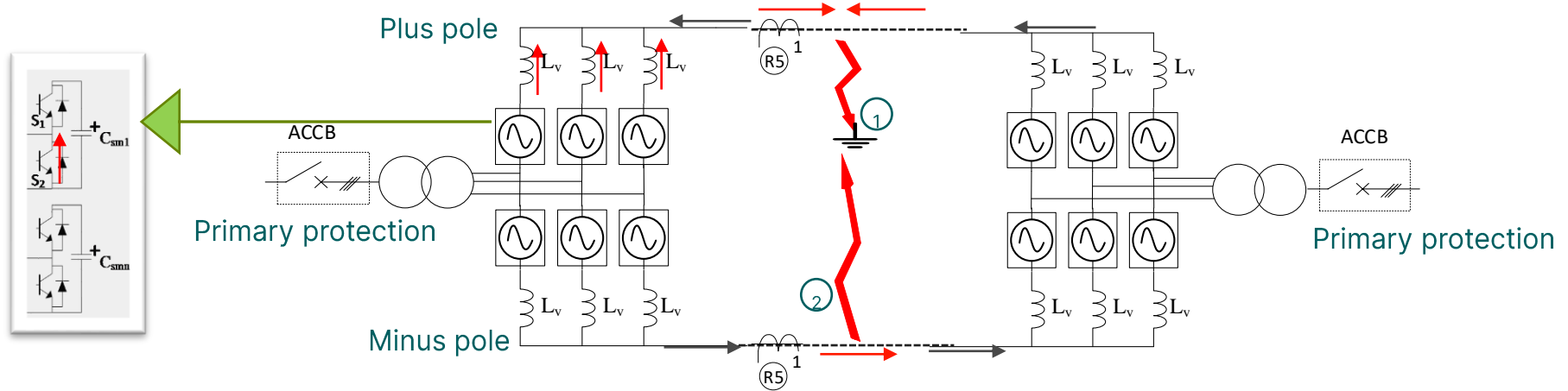
# AC protection approach – fault clearing


- S2 Diode Conducts
- Fault current uncontrolled




# DC faults clearing – point-to-point system

Valves are protected (e.g. by bypass thyristors)


### Fault 1: plus-pole to ground @ 3s

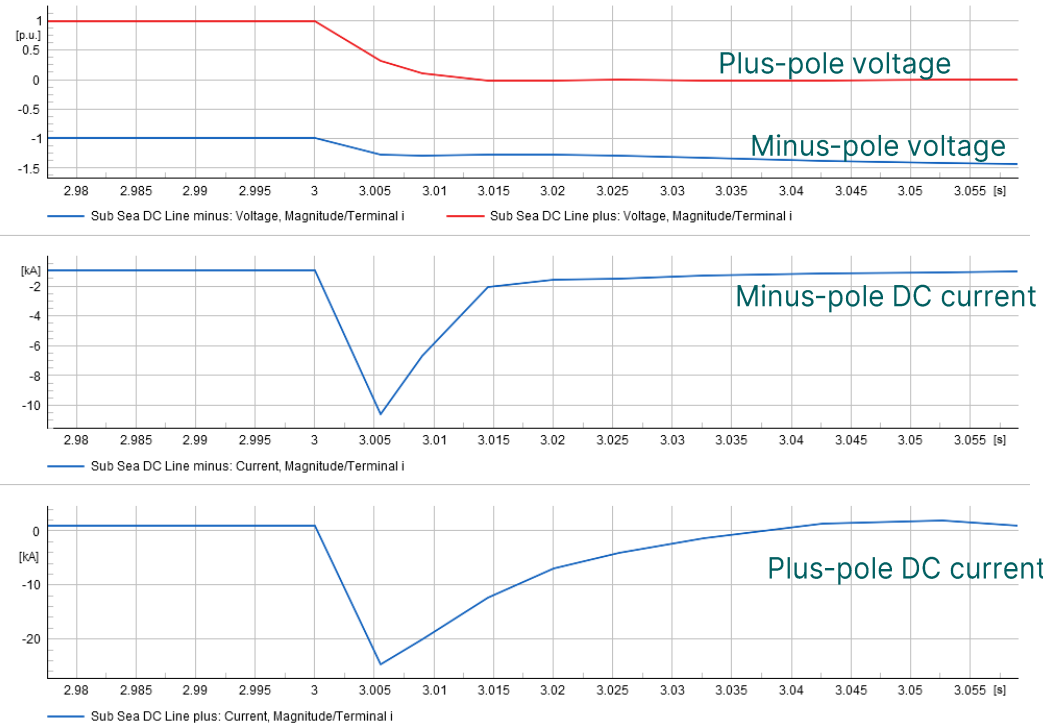
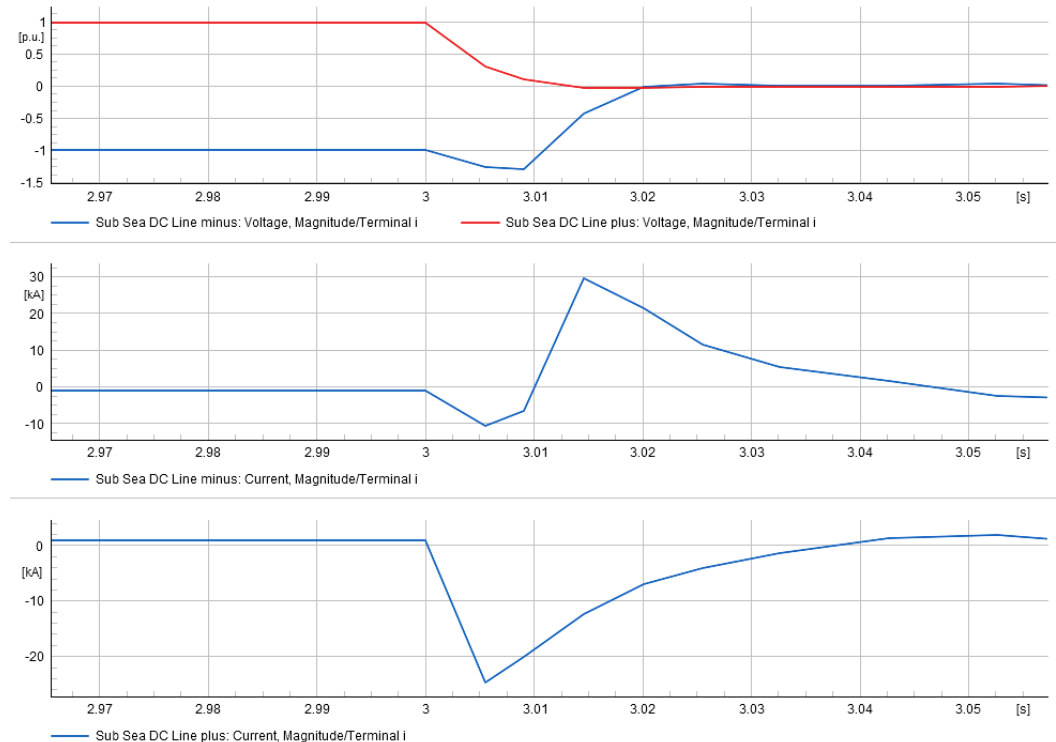
### Fault 2: fault 1 @3s + minus-pole to ground @ 3.01s





# HVDC grids - new requirements

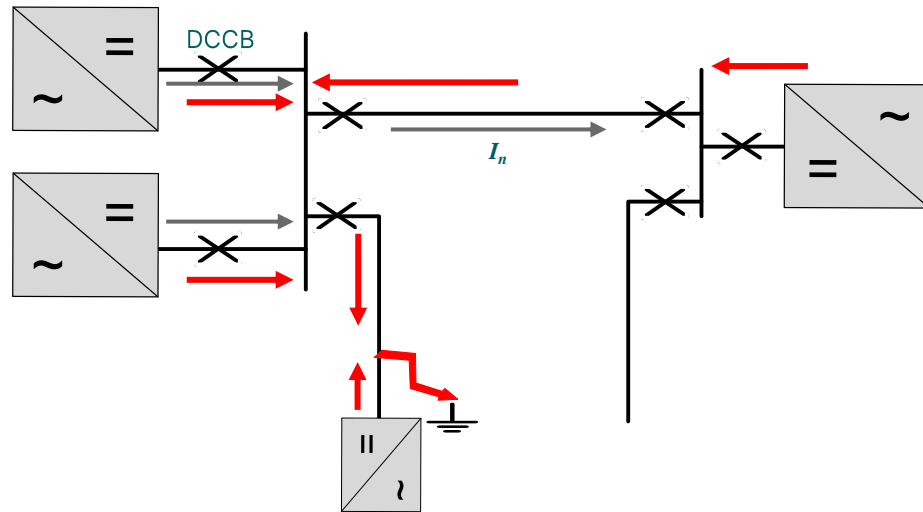



- With AC protection, a single DC fault trips the whole grid
- DCCB options:
  - Assuming DCCB everywhere
    - Discrimination – how to identify and isolate faulted section only
    - Breakers of different class/ different settings (line side/converter side)
  - Breakers at selected locations
    - Allow system split during faults

# DC protection approach to HVDC grids

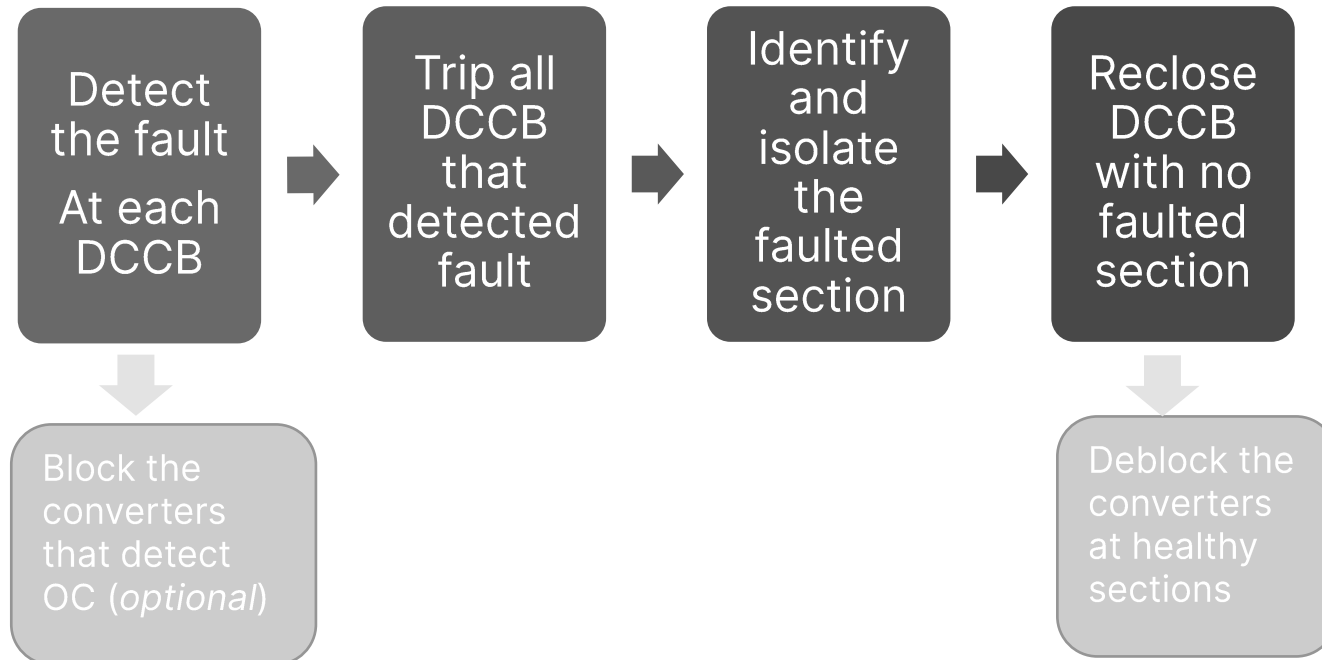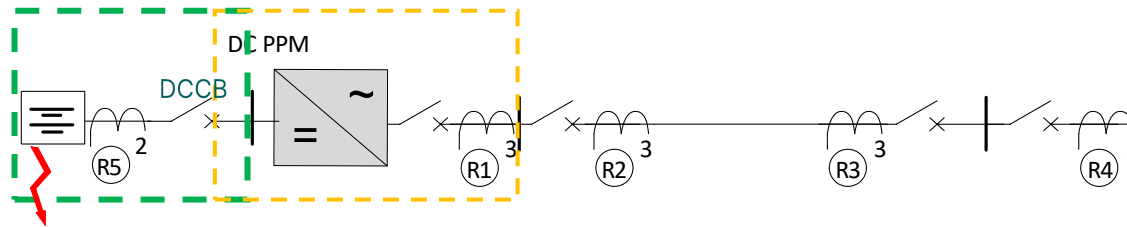



# DCCB – operating principle

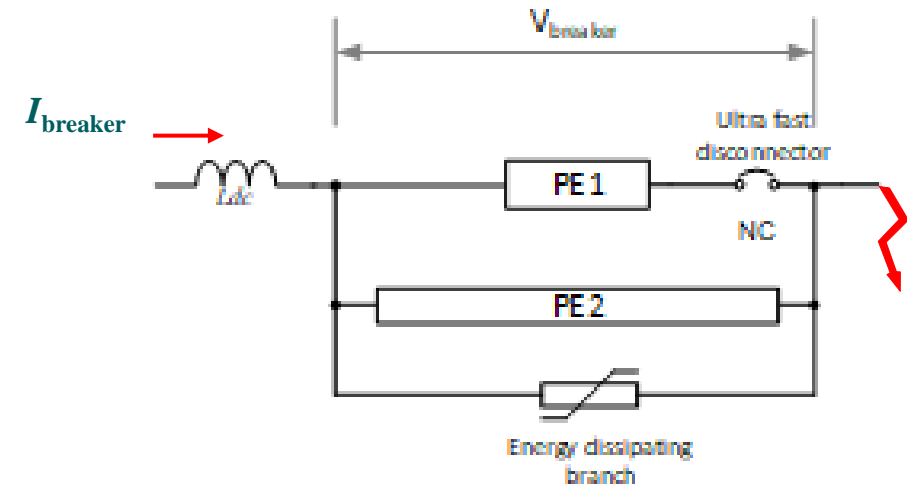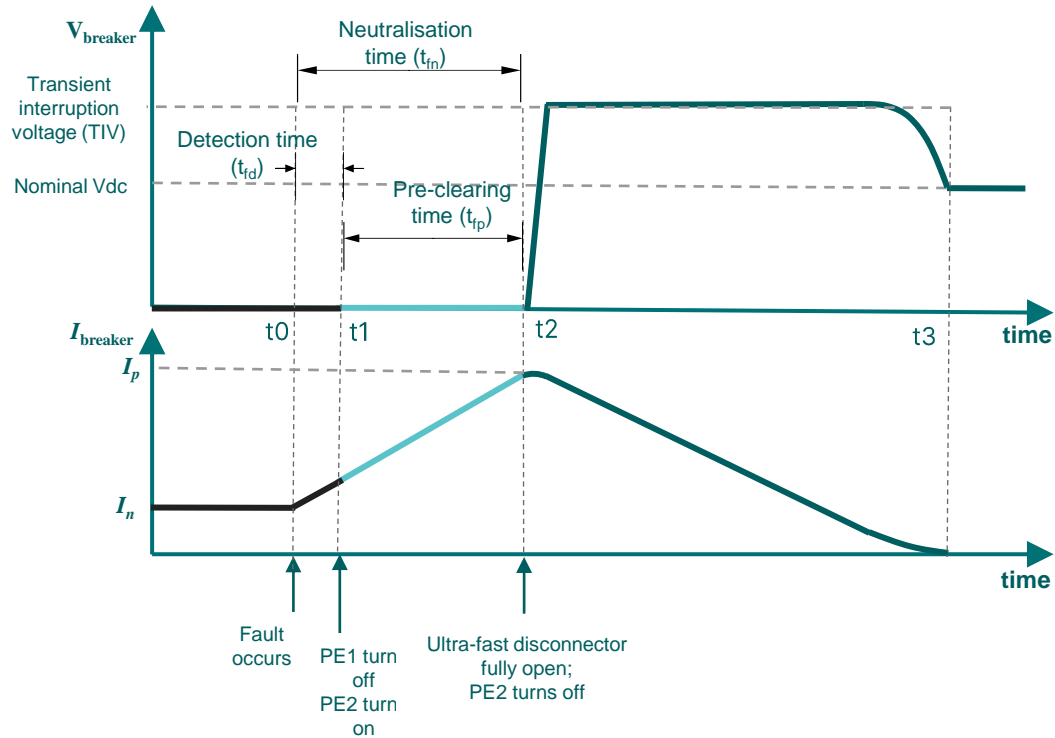

Hybrid DCCB

PE1 : main power electronics branch



PE2 : Current Commutation branch

# DCCB – operating principle

Current interruption requirement ( $I_p$ ) for the DCCB depends strongly on the neutralisation time ( $t_{fn}$ ) and inductance in the current fault path

Peak DCCB interruption current
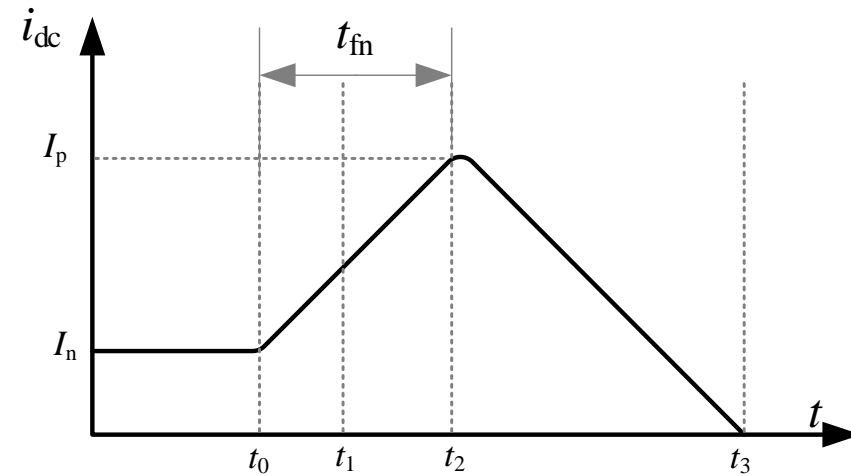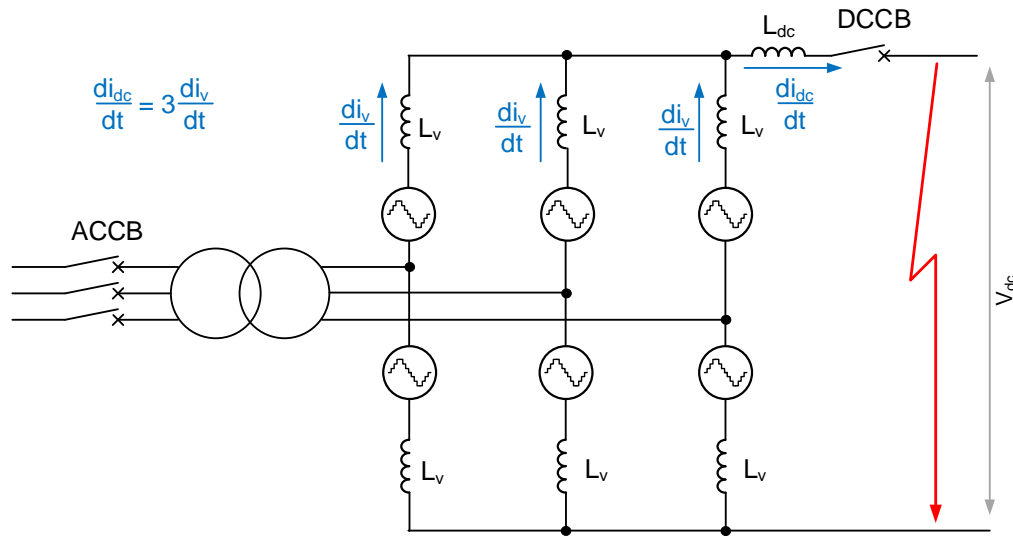
$$I_p = I_n + \frac{di_{dc}}{dt} \cdot t_{fn}$$




Initial di/dt in DCCB

$$\frac{di_{dc}}{dt} = \frac{V_{dc}}{L_{eff}}$$


$$L_{eff} = \left[ \frac{2 \cdot L_v}{3} + L_{dc} \right]$$
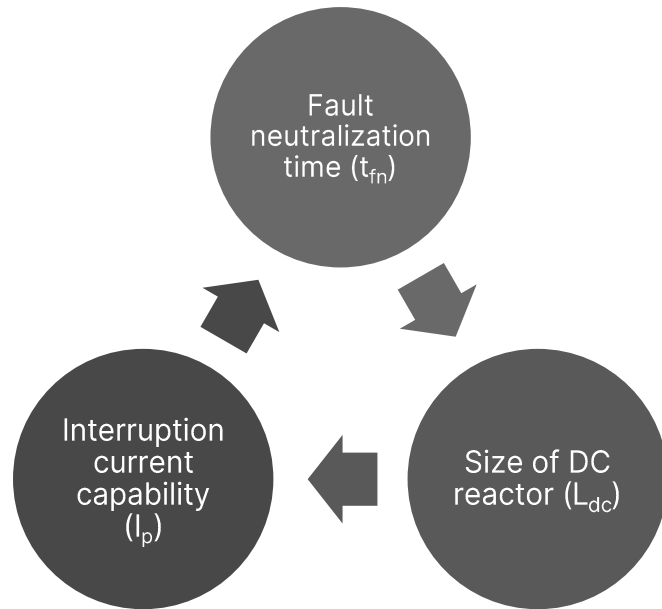
# DCCB design metrics

Three inter-dependent variables  
(for same  $I_n$ ,  $V_{dc}$ ,  $L_{circuit}$ )


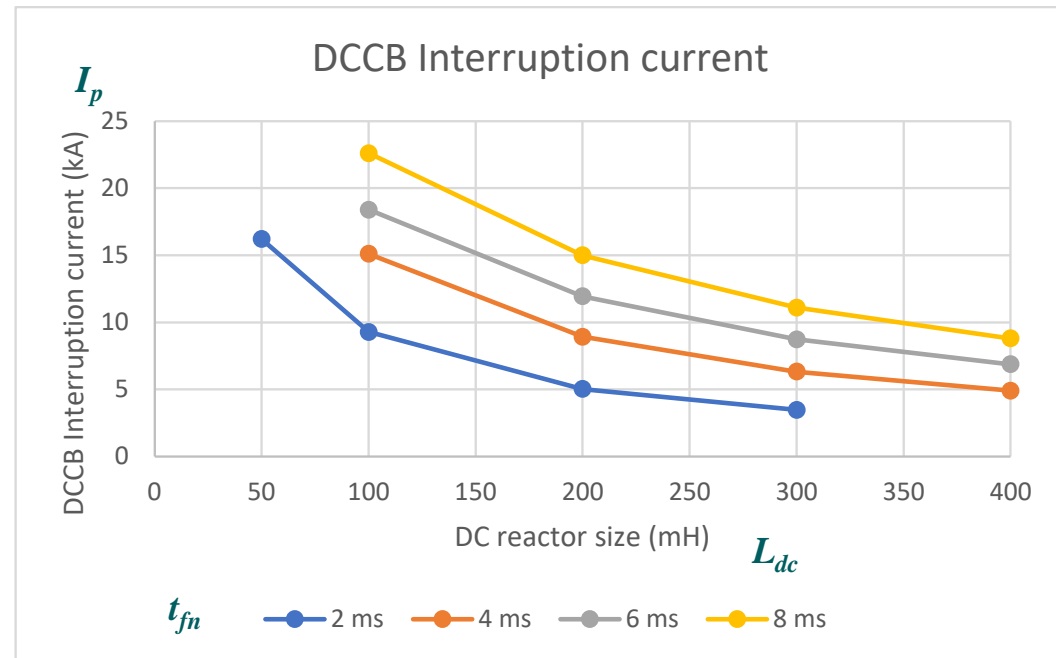
$$I_p = I_n + \frac{V_{dc}}{L_{dc} + L_{circuit}} \cdot t_{fn}$$




$I_n$  depends on the location of the breaker

$L_{circuit}$  is the dependent on the fault location

# DCCB design – impact of breaker location
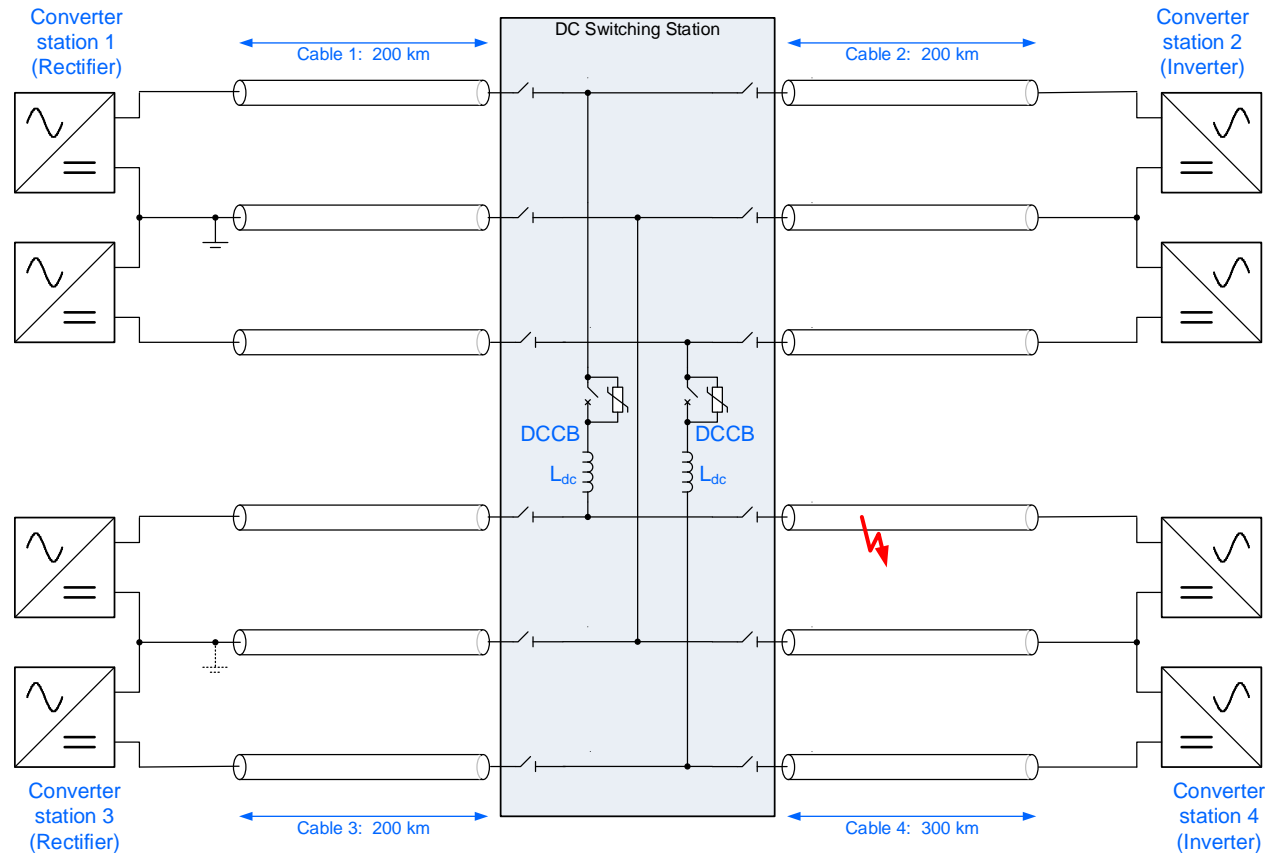
## Expansion of two independent bipoles using an intermediate DC Switching Station




- Lower  $I_p$  due to lower  $I_n$
- Cost-effective way of adding flexibility
- But DCCB is needed to prevent losing both bipoles for one fault.
- Only one DCCB and one DC reactor needed (per pole)
- Very simple protection strategy:
  - OC in DCCB → open DCCB
  - N-1 fault → AC protection approach


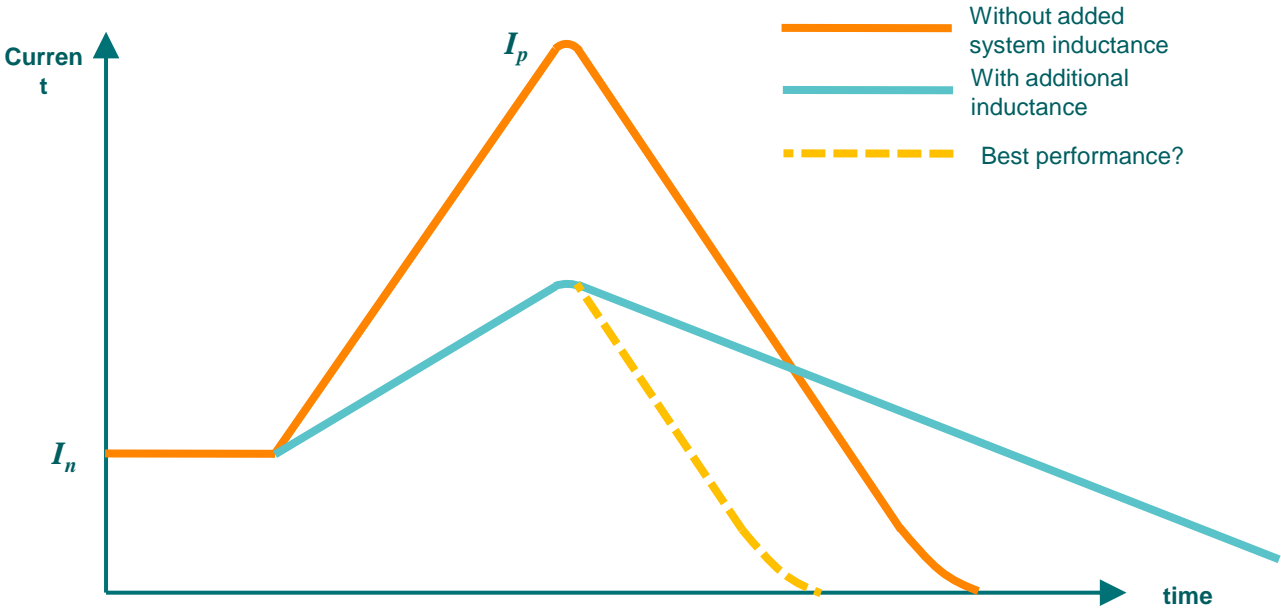
# DCCB design – impact of inductance

Higher inductance:

- Lower  $I_p$
- But slower current decay rate



# DCCB design – impact of fault location

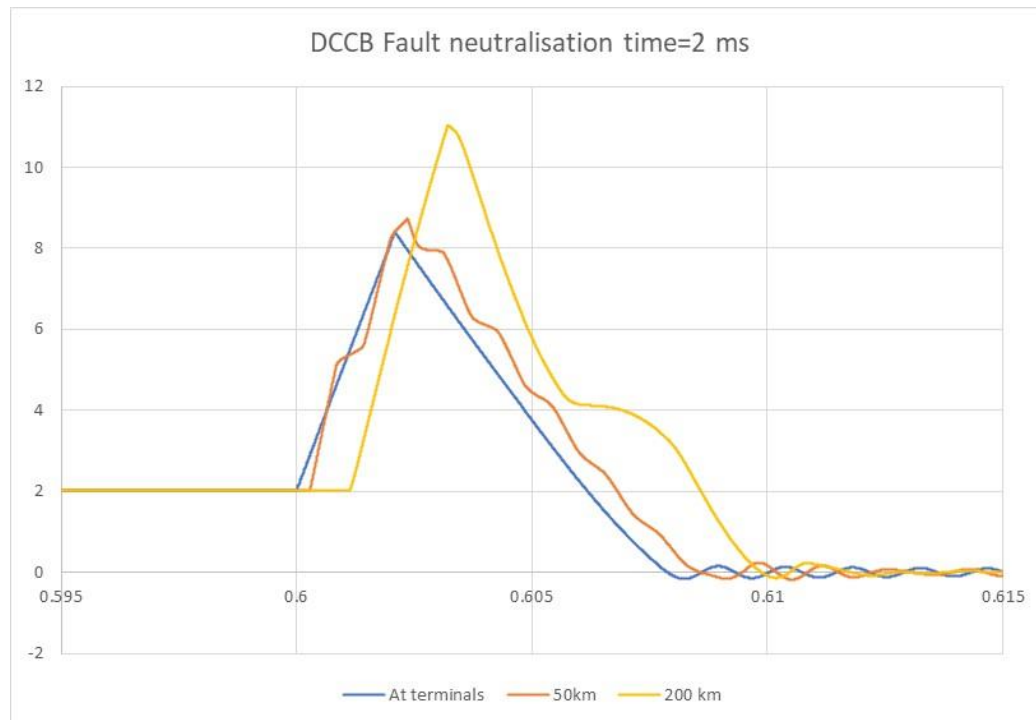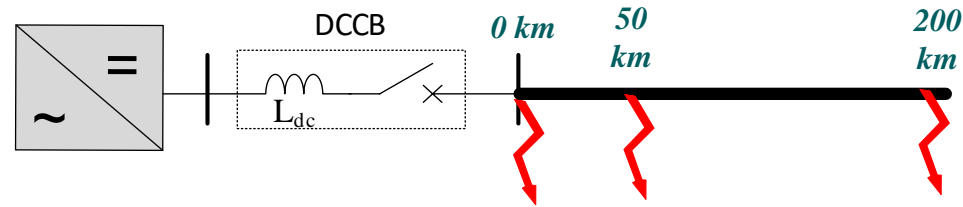

- Fault directly at converter station gives the expected response
- $I_p = 8.3 \text{ kA}$
- Faults at a distance from converter station give more complex results
- Reason: Reflection at cable/converter station boundary causes partial voltage reversal



$L_{dc} = L_v = 100 \text{ mH}$ . Expected initial  $di/dt = 3.14 \text{ kA/ms}$

# DCCB design – impact of cable type

Point-to-point case,  $f_n = 2$  ms

$\rho_{\text{sheath}} = 2.6 \times 10^{-8} \Omega \cdot \text{m}$  (Aluminium)

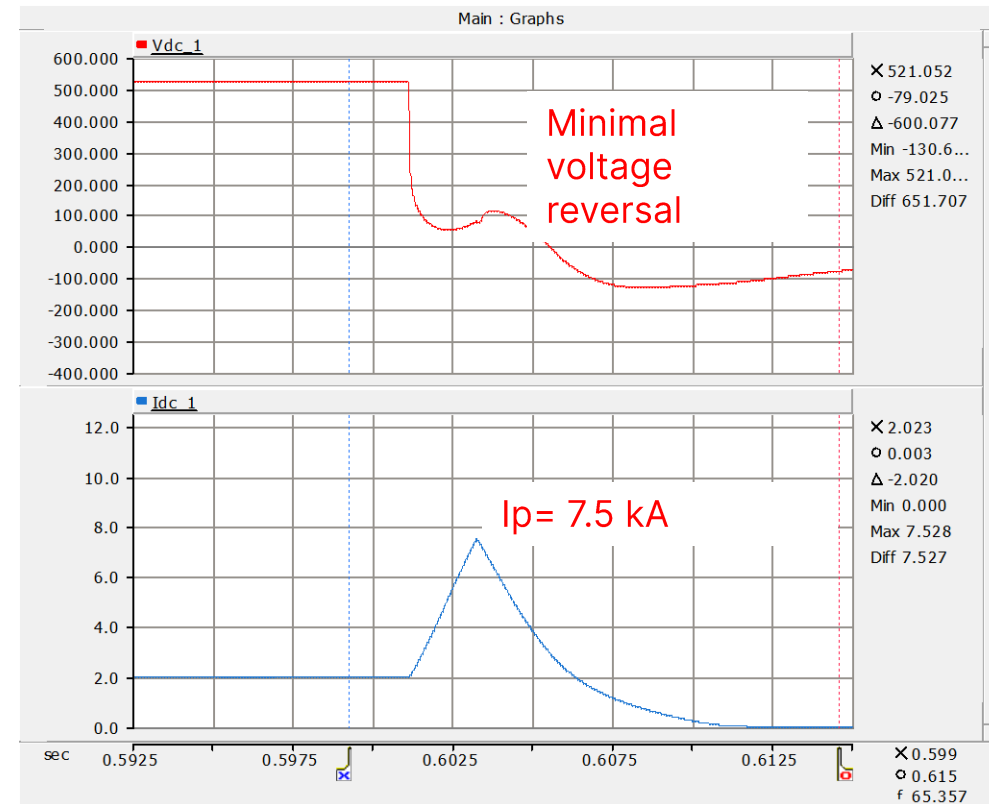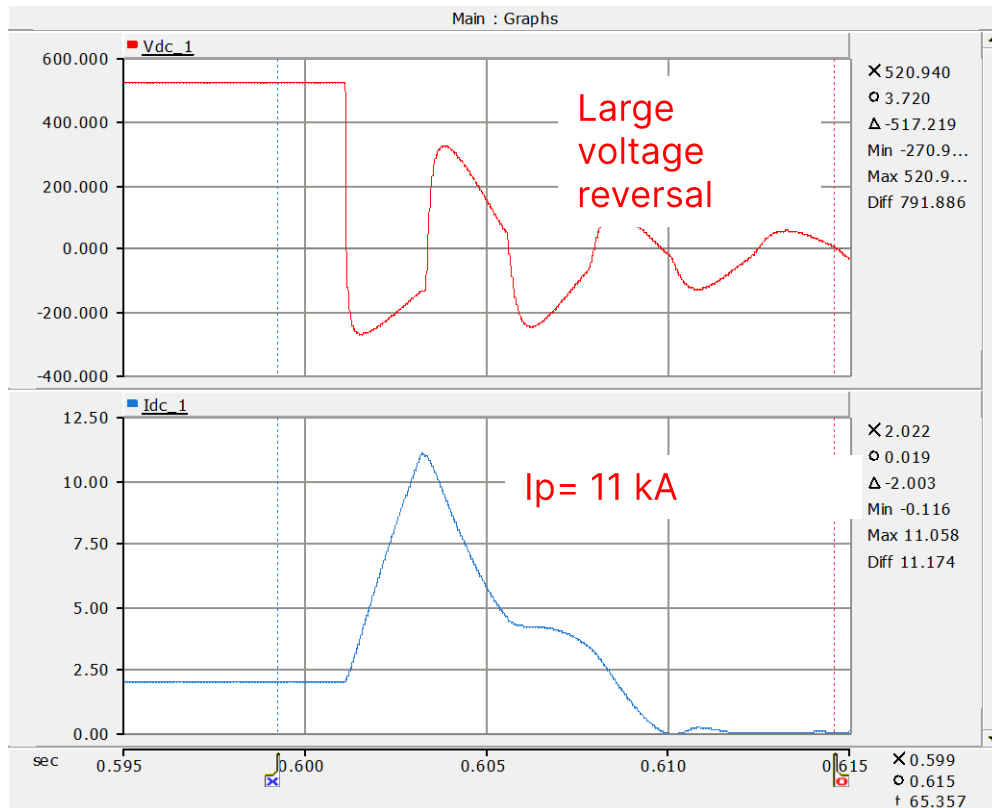$\rho_{\text{sheath}} = 2.2 \times 10^{-7} \Omega \cdot \text{m}$  (lead)




Simulations showed little influence from: Soil resistivity, Location of sheath earthing, Resistance of sheath earthing - BUT sheath resistivity has a very big effect
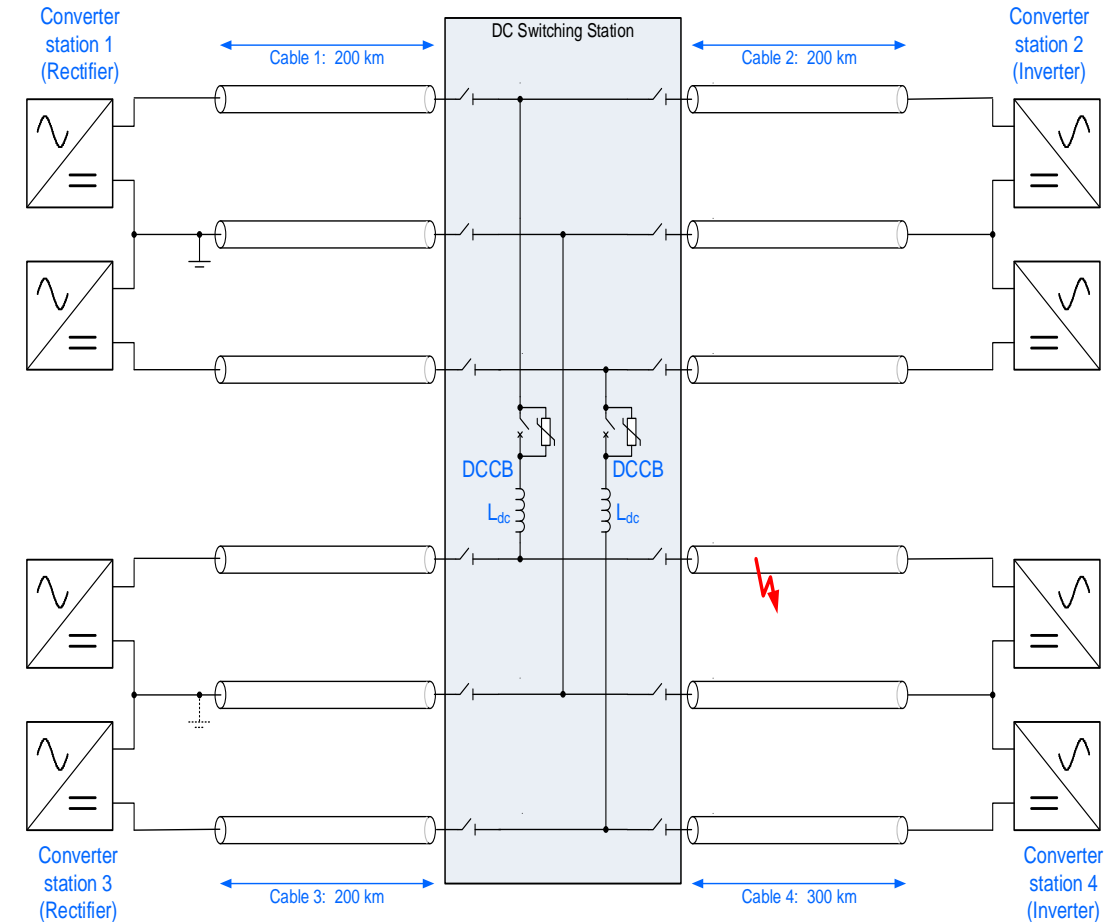
# DCCB design – impact of remote converters mode of operation

Two main options for converters 1 and 2 (healthy converters)


- Remote converters remain deblocked
  - Valve currents must remain within the SOA for the IGBTs.
  - DC reactor must be increased until this condition becomes true.
  - Typical manufacturer recommendation is:
    - $SOA < 2 \times$  rated current
    - This corresponds to  $4 \times$  rated DC current, –i.e. DC bus current of 8 kA
- Remote converter temporarily blocks during fault clearing
  - System will experience a loss of power for a short period of time
- Impact on Fault ride through requirements and performance






# DCCB design – Impact of remote converters mode of operation

### Converters block during the fault

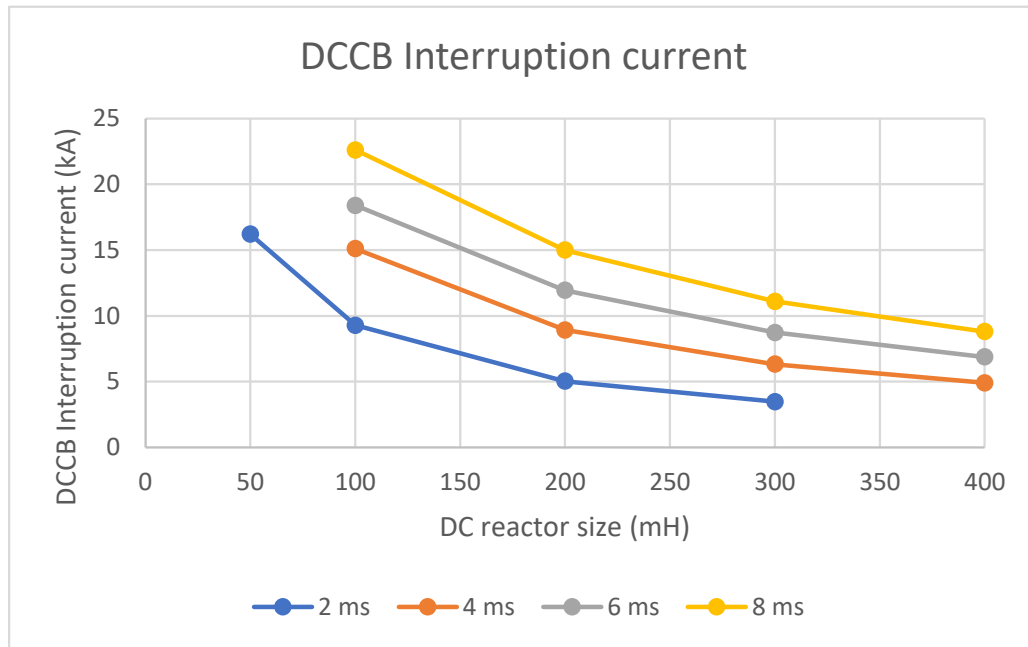
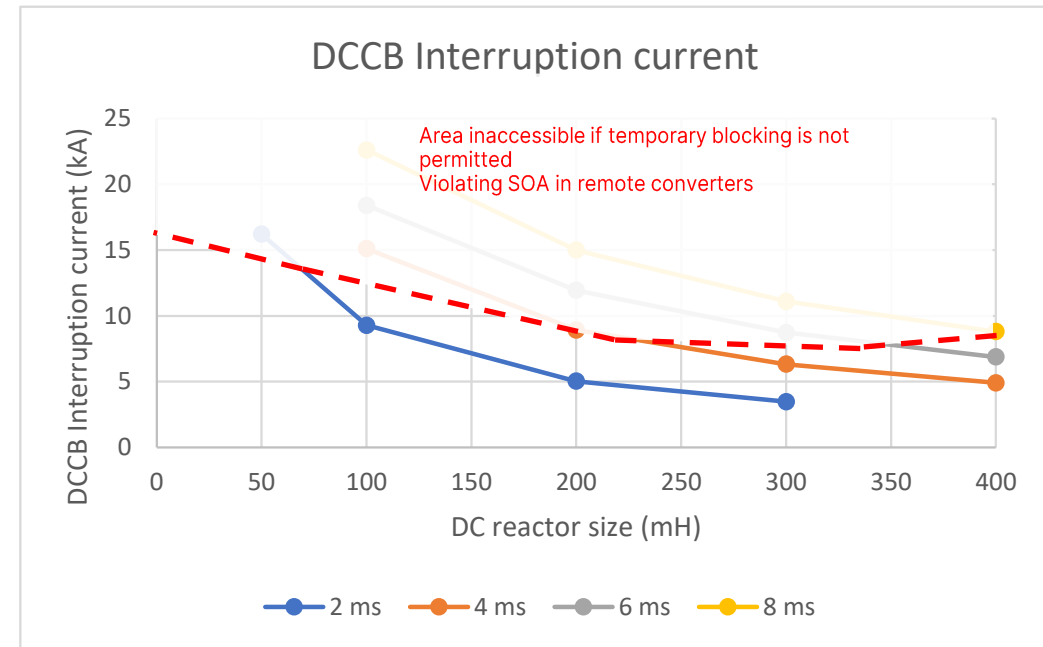
### Converters are deblocked during the fault



# Conclusions

- DC grids are emerging due to the requirements for cost effective solutions for deep electrification esp. offshore.
- Subsystems designs have been carried out during the last decade
  - EC Twenties project concluded in 2013 - GE prototype of a hybrid DCCB
- Regardless of the breaker technology, the design metrics (mainly three) are interdependent
  - Current interruption capability
  - Fault neutralization time
  - Breaker inductance
- They are impacted by:
  - Breaker location in the DC Grid
  - Cable type
  - Allowed mode of operation of converters during a DC fault (block/remain deblocked)
  - Effective fault inductance
- Different DC breaker classes might need to exist to cover the evolution of DC Grids